

Electrical Power Engineering (2)

Code: EP2207

Lecture: 4

Tutorial: 4

Total: 8

Dr. Ahmed Mohamed Azmy

Department of Electrical Power and Machine Engineering

Tanta University - Egypt




Faculty of
Engineering



Tanta University

Experimental Determination of the General ABCD Constants of TLs

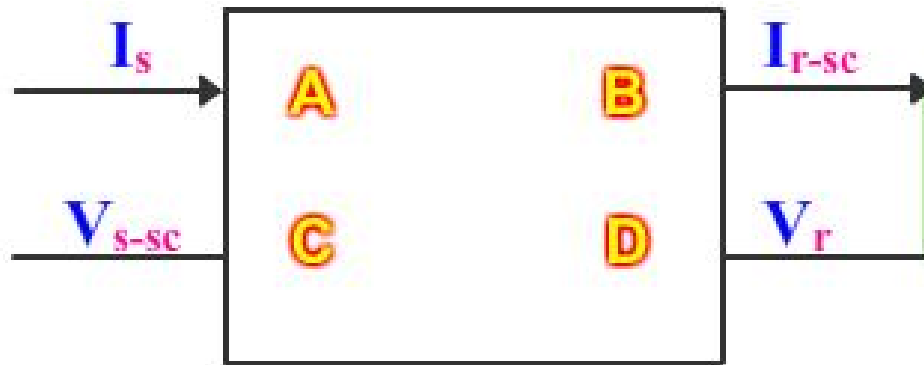Short circuit on the receiving-end of transmission line



$$B = \frac{V_{s-sc}}{I_{r-sc}}$$


$$V_s = AV_r + BI_r \longrightarrow V_{s-sc} = BI_{r-sc}$$

$$I_s = CV_r + DI_r \longrightarrow I_{s-sc} = DI_{r-sc}$$

$$D = \frac{I_{s-sc}}{I_{r-sc}}$$

Experimental Determination of the General ABCD Constants of TLs

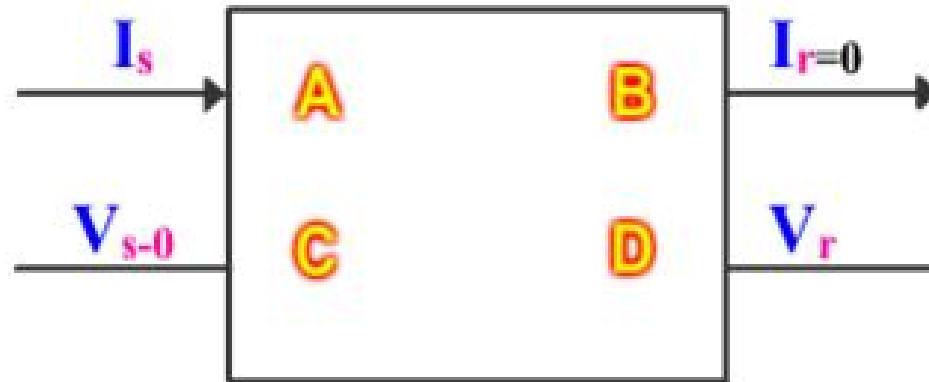Open circuit on the receiving-end of transmission line



$$A = \frac{V_{s-0}}{V_{r-0}}$$

$$V_s = AV_r + BI_r \longrightarrow V_{s-0} = AV_{r-0}$$

$$I_s = CV_r + DI_r \longrightarrow I_{s-0} = CV_{r-0}$$

$$C = \frac{I_{s-0}}{V_{r-0}}$$

Power Circle Diagrams

The following equations determine the current and voltage at any point on a given transmission line

$$V_s = V_r \cosh(\theta) + I_r Z \frac{\sinh(\theta)}{\theta}$$

$$I_s = I_r \cosh(\theta) + V_r Y \frac{\sinh(\theta)}{\theta}$$

$$V_r = V_s \cosh(\theta) - I_s Z \frac{\sinh(\theta)}{\theta}$$

$$I_r = I_s \cosh(\theta) - V_s Y \frac{\sinh(\theta)}{\theta}$$

Power Circle Diagrams

For balanced conditions, the current and voltage at one end of the transmission line can be expressed as a simple linear function of the current and voltage at the other end

$$V_s = A V_r + B I_r$$

$$I_s = C V_r + D I_r$$

$$V_r = D V_s - B I_s$$

$$I_r = A I_s - C V_s$$

Power Circle Diagrams

Current and voltage at one end of the TL can be expressed as functions of current and voltage at the other end

Notice : The general line constants (A, B, C and D) are all complex quantities and each have both magnitude and direction. Assume that:

$$A = A \angle \alpha \qquad B = B \angle \beta$$

$$C = C \angle \gamma \qquad D = D \angle \delta$$

$$V_r = D V_s - B I_s$$


$$I_r = A I_s - C V_s$$

$$V_s = A V_r + B I_r$$

$$I_s = C V_r + D I_r$$

Receiving-end Power Circle

$$V_s = A V_r + B I_r$$

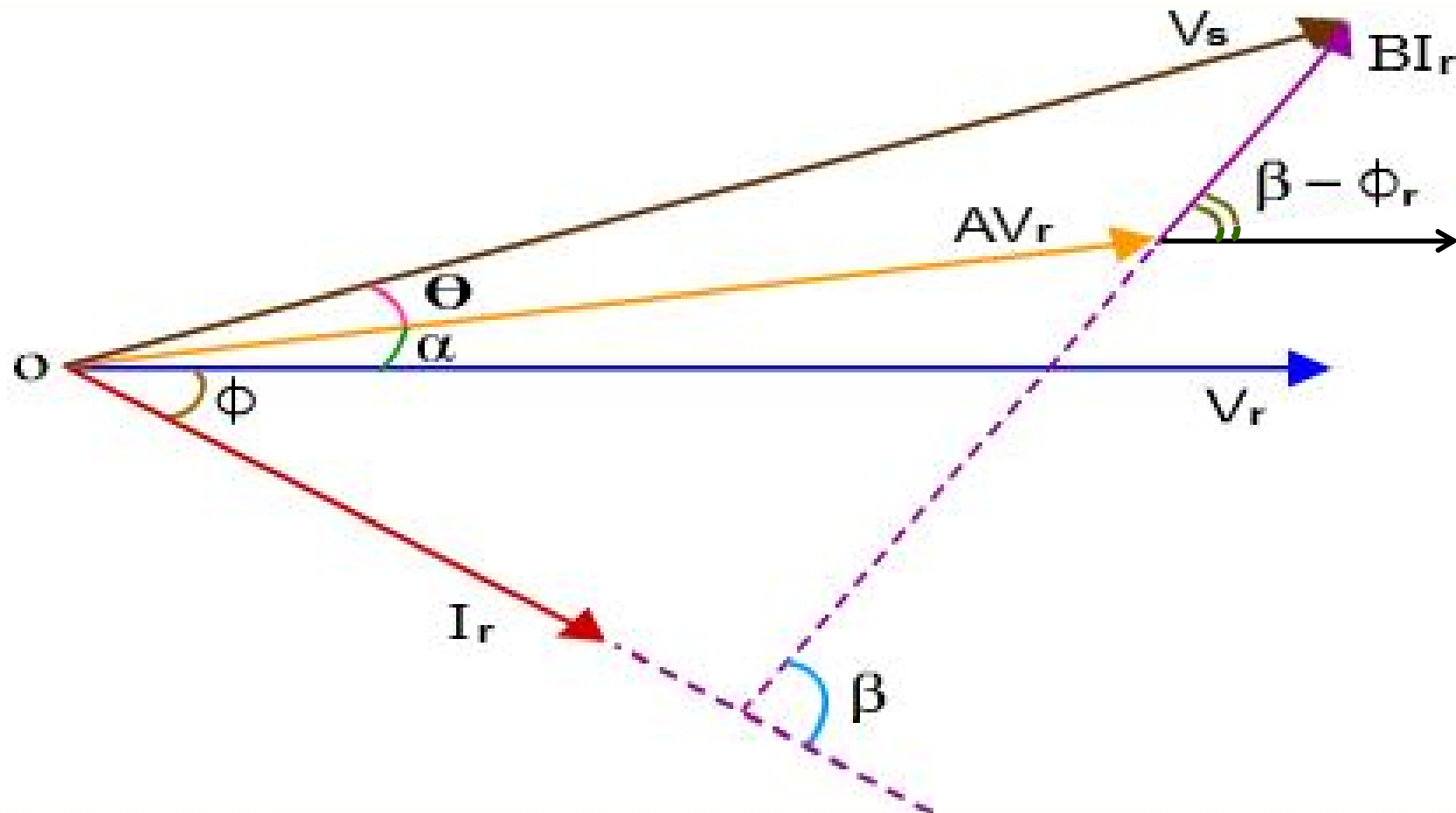


Receiving-end Power Circle

This diagram can be modified by dividing each vector by the complex quantity B


Regarding the magnitudes, it is enough to change the scale of the diagram

The diagram has to be rotated through an angle $-\beta$ (i.e. clockwise)

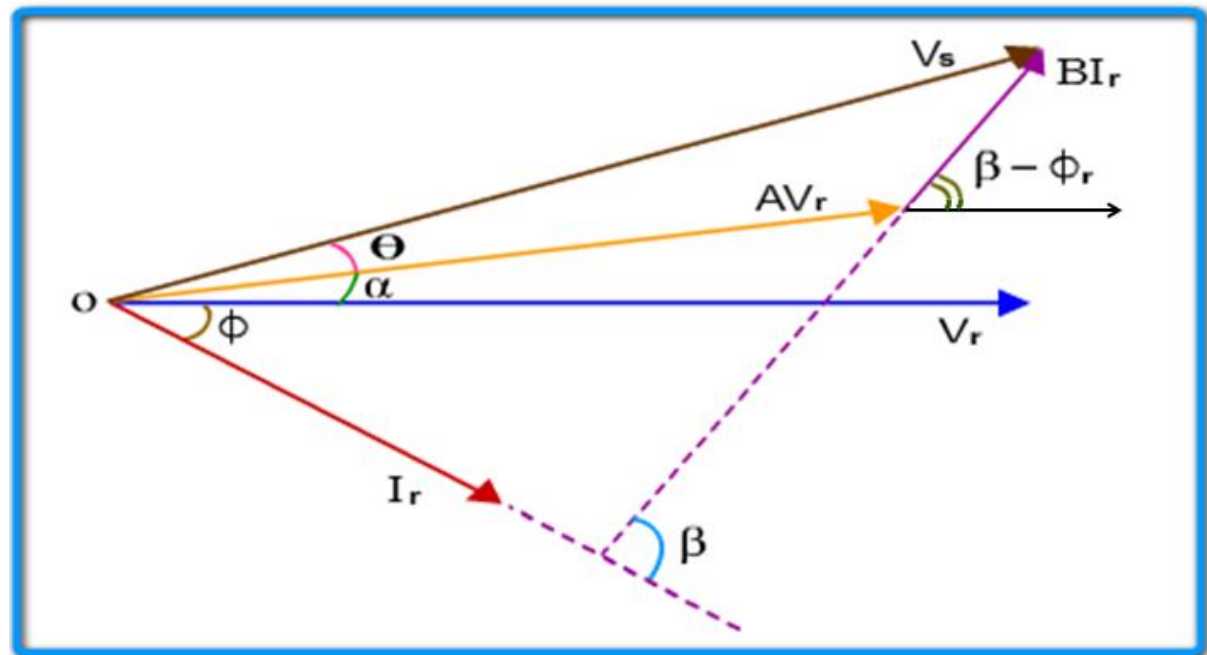
The active component of receiving-end current, i.e. $I_r \cos(\phi_r)$, is aligned with the reference vector




Receiving-end Power Circle

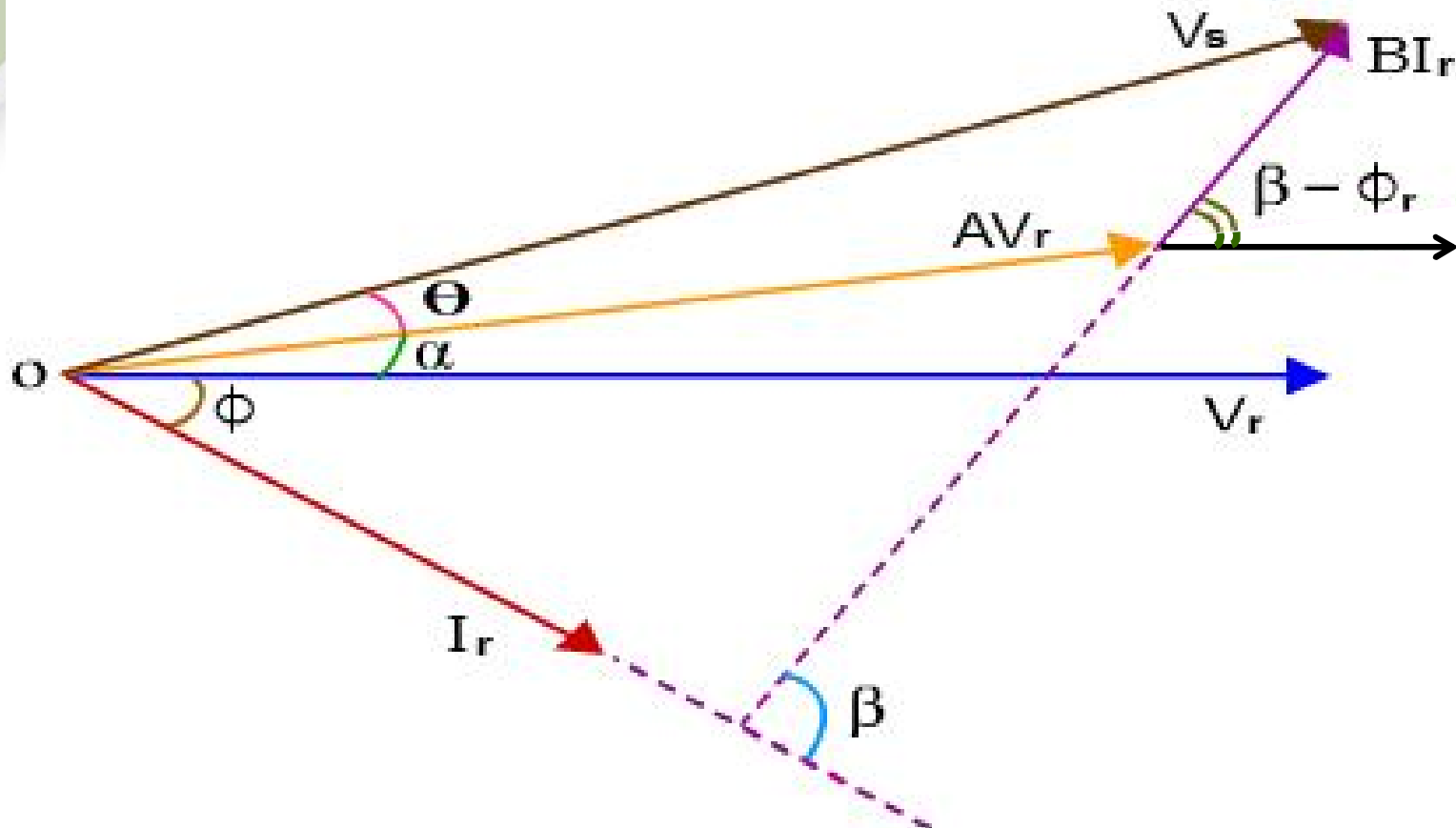


Receiving-end Power Circle

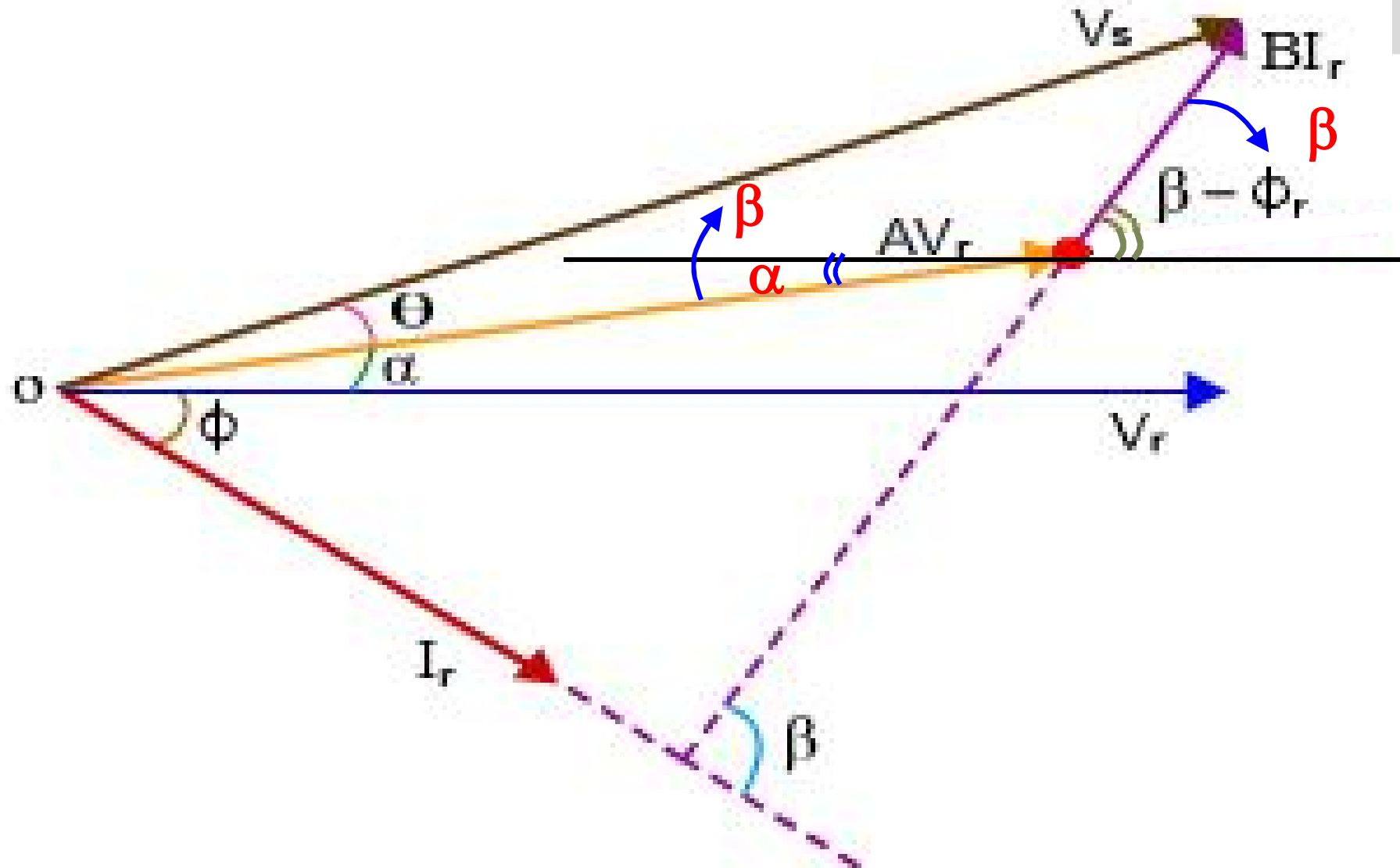


Receiving-end Power Circle

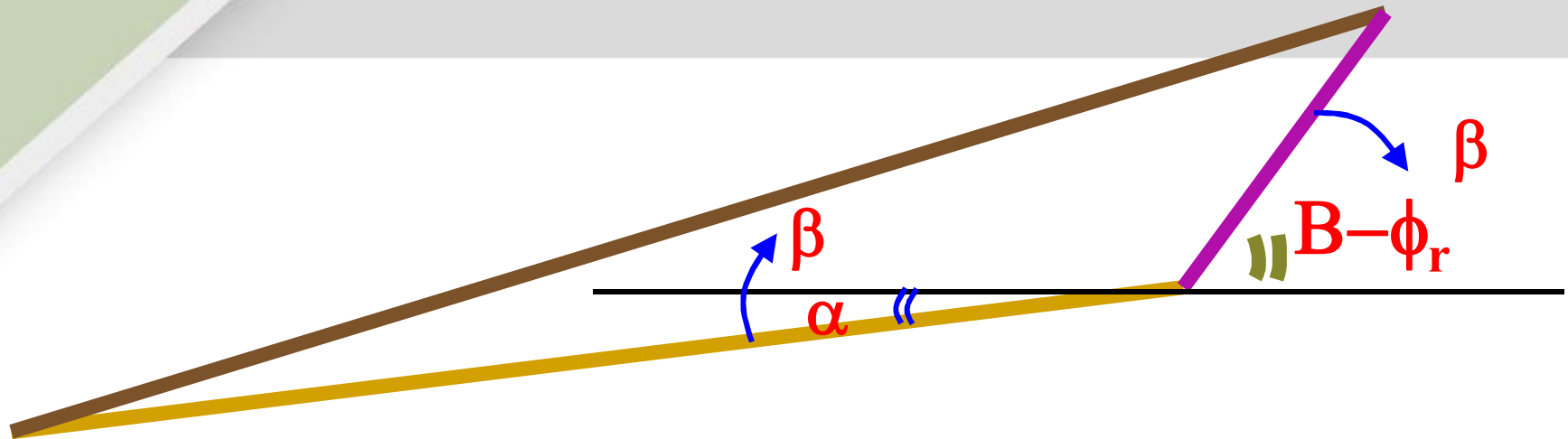


Receiving-end Power Circle

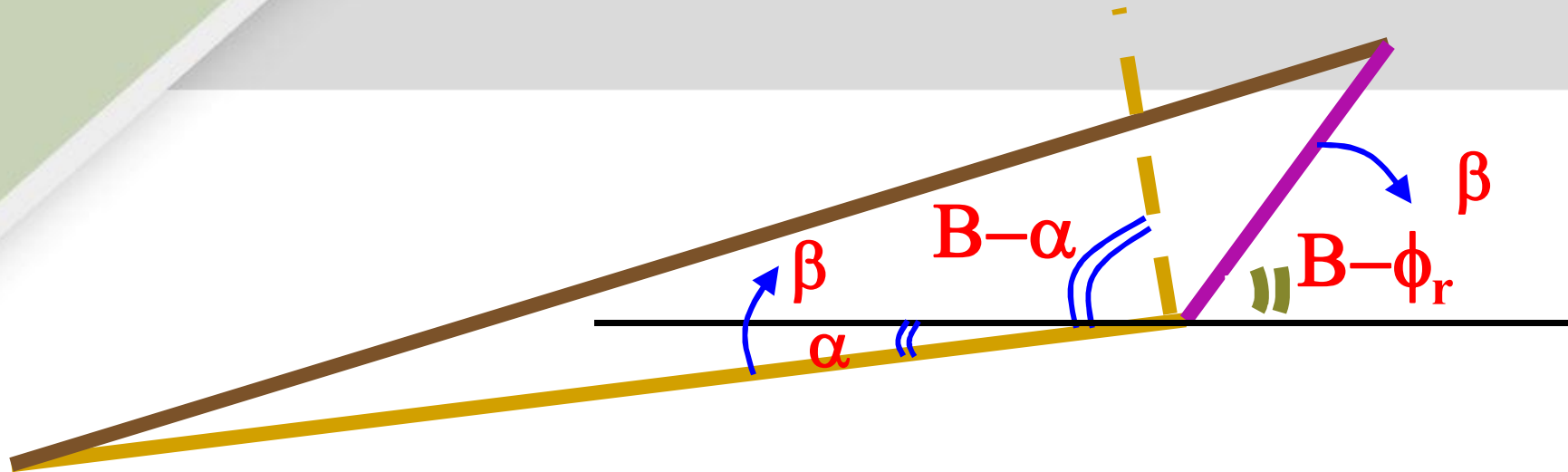


Receiving-end Power Circle

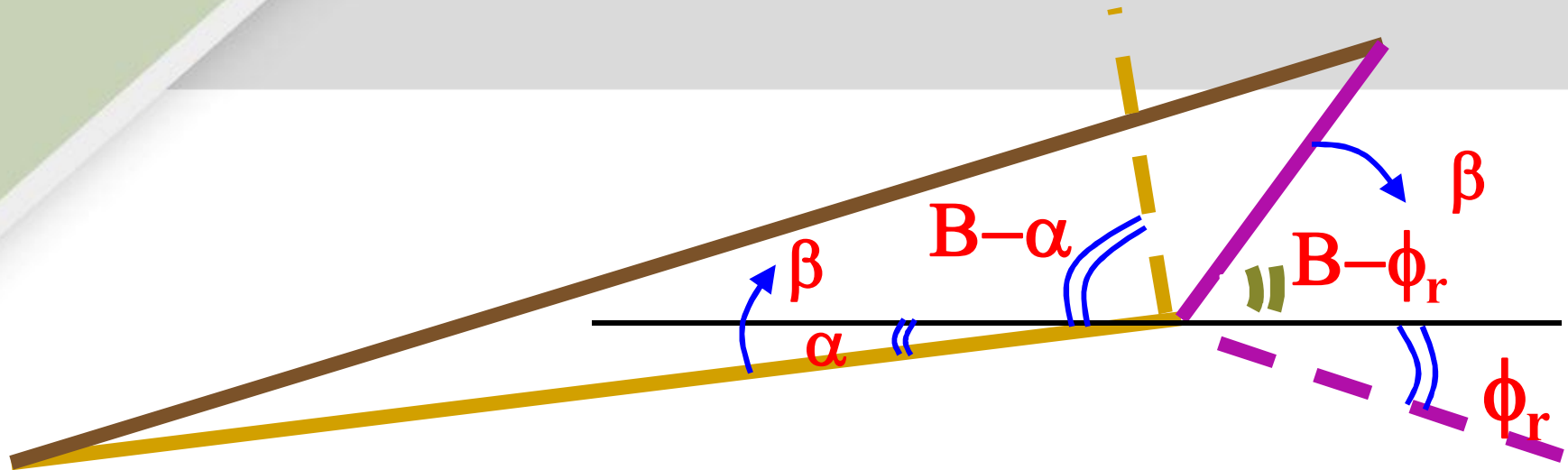


Receiving-end Power Circle

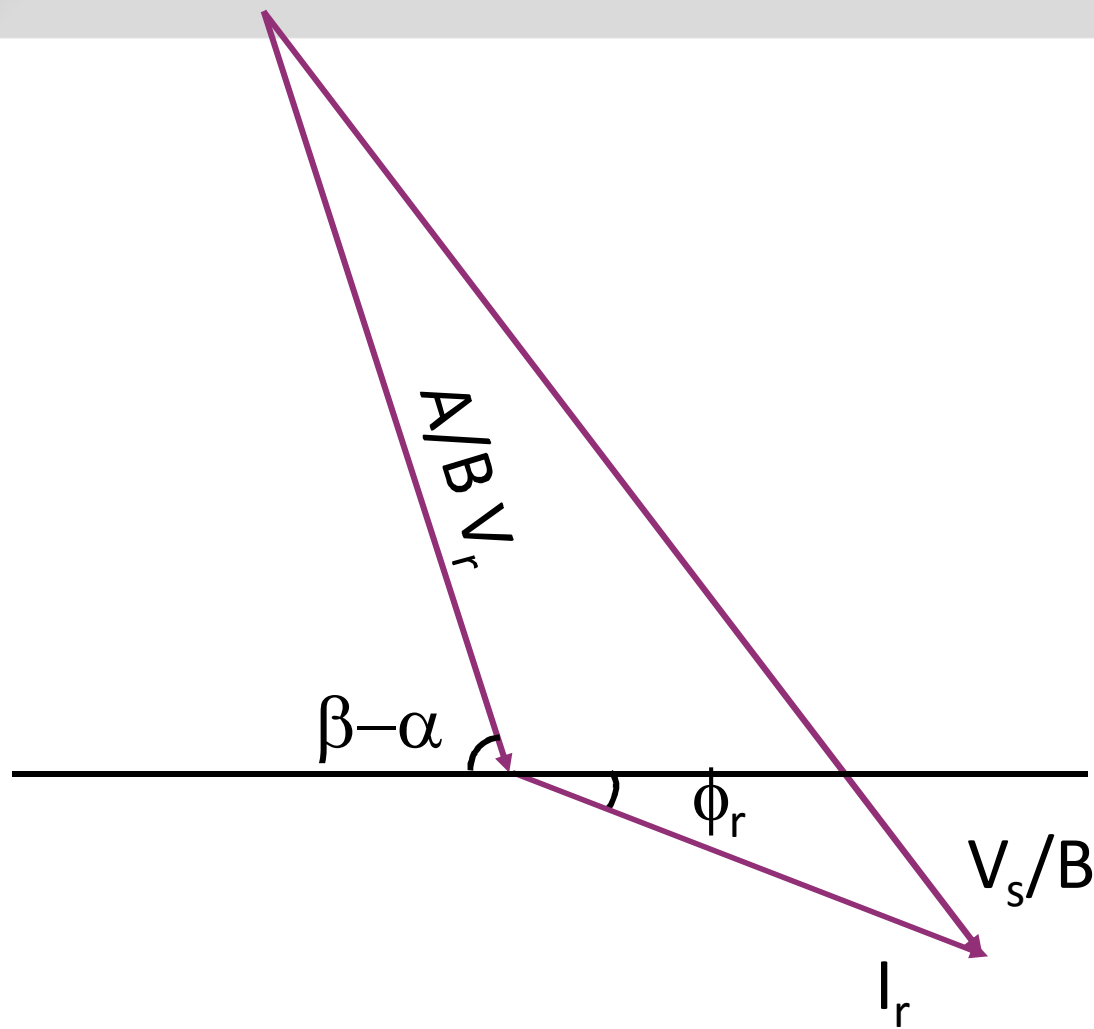

Receiving-end Power Circle

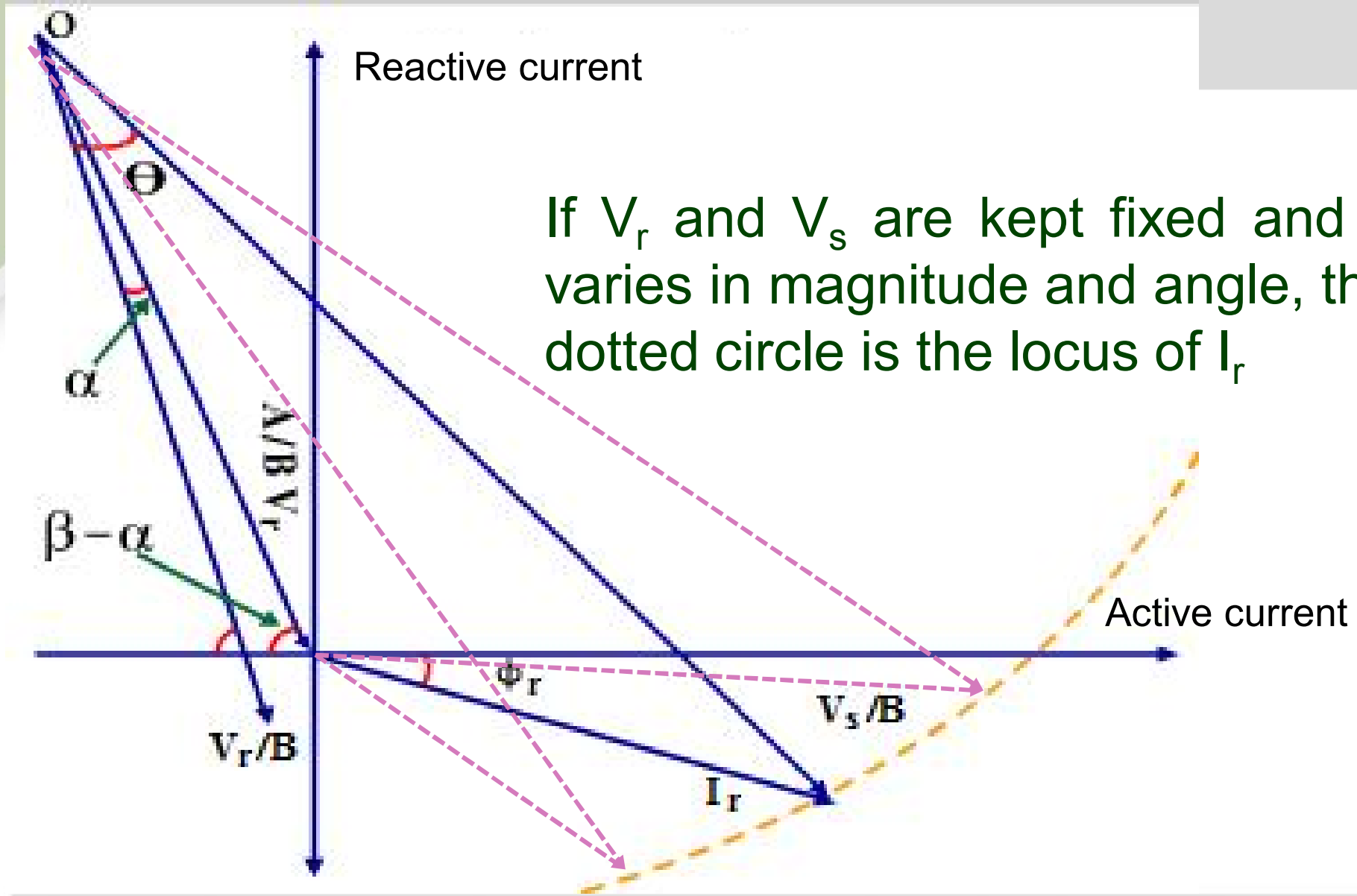

Receiving-end Power Circle

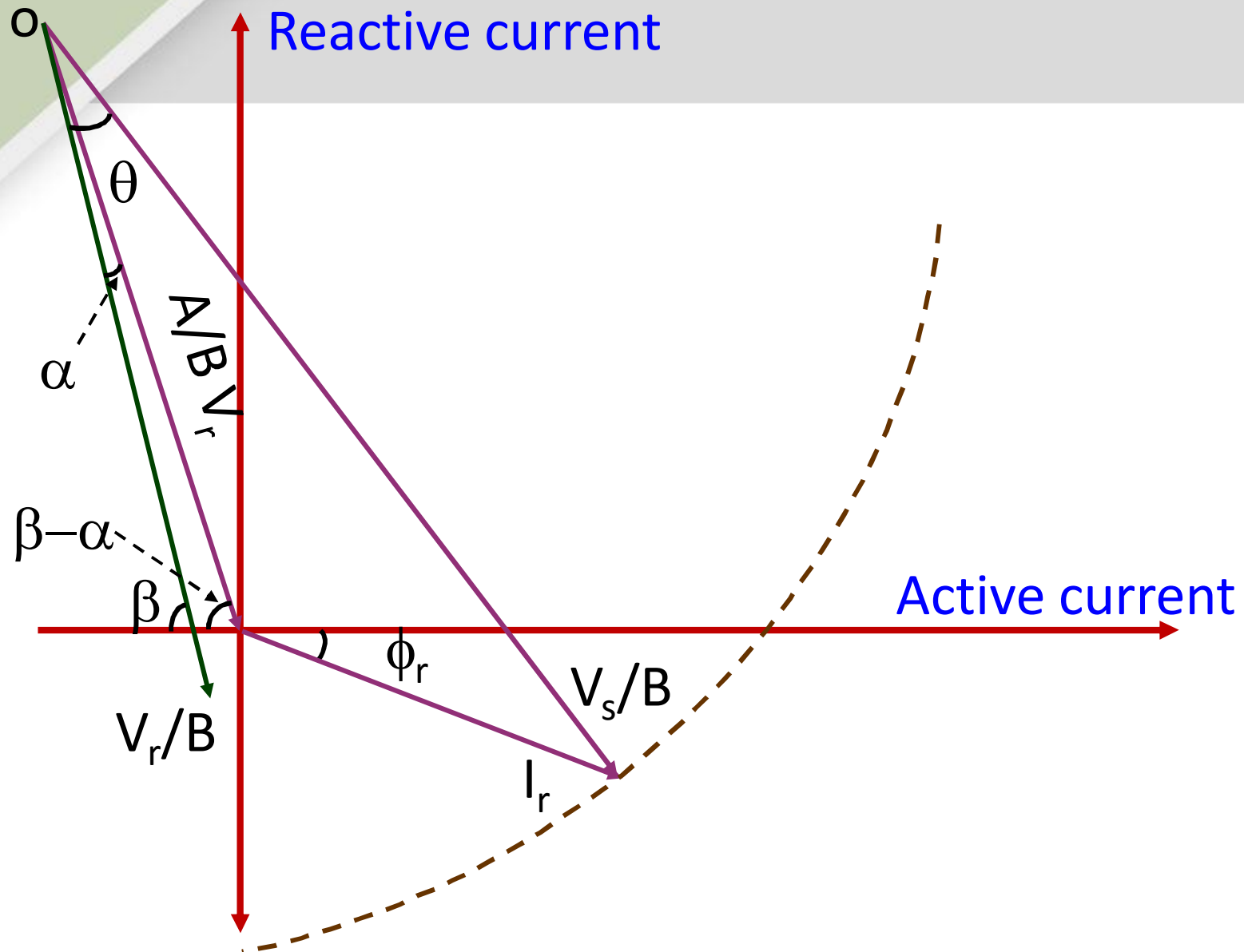

Receiving-end Power Circle

